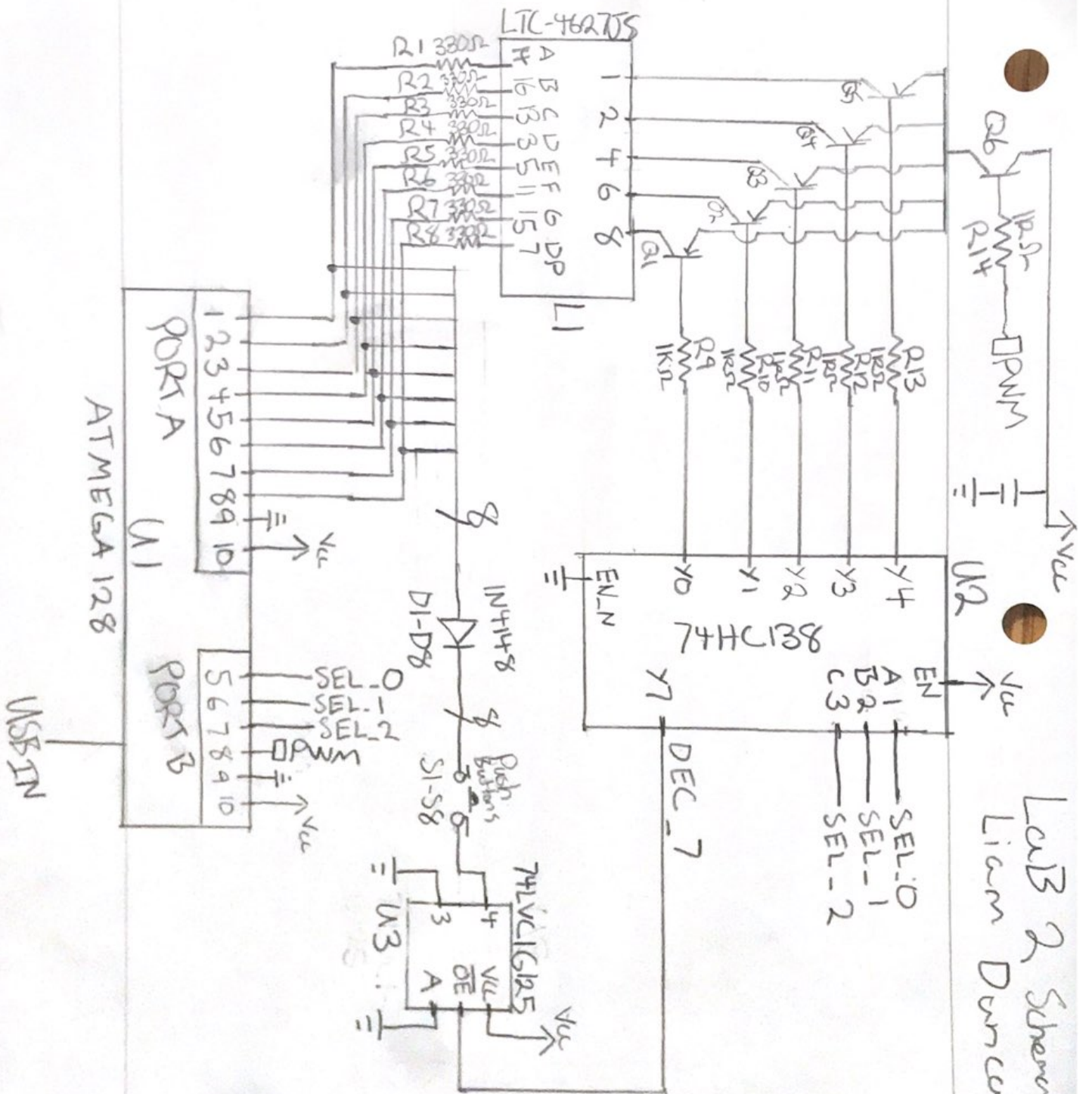


Lab 2 Scheutic  
Liam Duncan



## a) LED Segment Resistor Calculations

Resistor options are  $330\Omega$ ,  $1k\Omega$ , or  $10k\Omega$

According to Atmega28 datasheet,

I/O pins output high Voltage is minimum  $4.2V$

Max current per pin is  $40mA$

Max current per segment in LED display is  $25mA$  and  $40mW$

Assuming Atmega is sending a max of  $5V$  and we want current to equal  $20mA$

So it is not at max

$$\text{So, } V=IR \quad R = \frac{V}{I} = \frac{5}{20 \times 10^{-3}} = 250\Omega \quad \text{Our}$$

Closest Resistor is  $330\Omega$

this will give us  $\frac{V}{R} = I = \frac{5}{330} = 15mA$

which is a good safe current number.

This also gives us some slack the resistor could be smaller.

b) You know the light will be visible because according to the LT-4627DS Datasheet, at 15mA, the Relative luminous intensity is 1.5 which is visible by human eye.

c) Calculate Base resistor

From 74HC138 Datasheet  
Output Voltage is 4.5V

Assume  $I_c = 120\text{mA}$ , so  $hFE = 100$

$$I_b = \frac{120\text{mA}}{100} = 1.2\text{mA}$$

$$R_B = \frac{4.5 - .95}{1.2 \times 10^{-3}} = 2958\Omega$$

Pick closest option  $1k\Omega$

Connect Tri-state Buffer enable to 74HC138 Y7 output so that it is only enabled when A, B, and C are high. tie 1v1 to ground.